

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA
School of Electronics & Communication Engineering
B. Tech. 2nd Semester ECE / Backlog Major Examination (Even) 2024-25

Entry No: **24 BEC 055**

Total Number of Pages: [02]

Date:

Total Number of Questions: [07]

Course Title: Solid State Device (ECL DC 102) / Basic Electronics (ECL 1010)

Time Allowed: 3 Hour

Max Marks: [40]

Instructions / NOTE:

- i. Attempt all questions.
- ii. Assume an appropriate data / information, wherever necessary / missing.
- iii. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- iv. Important values: k (Boltzmann Constant) = 1.38×10^{-23} J/K; e (charge on an electron) = 1.6×10^{-19} C; ϵ_s (permittivity of Silicon) = 8.85×10^{-14} F/m .


Section A (2×5=10 Marks)

Q1.	<p>(a) Draw the exact output wave for the following given input.</p> <p>A circuit diagram showing a Si diode connected in series with the input source V_{in}. The diode is connected to ground. A load resistor R_{load} is connected between the output node and ground. The output voltage V_{out} is indicated across the load resistor. A small sketch of a waveform is shown next to the output node.</p>	[CO2]
	<p>(b) (i) If a reverse saturation current of a pn-junction diode is $25 \mu\text{A}$ at 20°C. Then what will be its value at 50°C? (ii) Why input impedance of a MOS device very high?</p>	[CO2]
	<p>(c) A 20 V peak-to-peak sine wave of 50 Hz is applied to the input of half-wave rectifier using a pn-junction diode of forward bias resistance of 50 ohms. Calculate the DC output power delivered to the load of 2.5 KOhms.</p>	[CO2]
	<p>(d) If CE current gain of a given BJT device is 50. Then find the value CB current gain of this BJT device.</p>	[CO3]
	<p>(e) (i) Define relation / expression of all the three stability factors used during biasing a BJT. (ii) Draw the circuit diagram of Voltage doubler circuit and explain its working.</p>	[CO3]

Section B (6-Questions of 5 Marks Each)

Q2.	<p>(a) Define Fermi-level and Fermi-Dirac distribution function. (02 Marks) (b) What is Hall Effect? Explain with diagram. Derive the relation of Hall Voltage (V_H) of a n-type semiconductor. (03 Marks)</p>	[CO1]
Q3.	<p>(a) Draw and explain the construction of n-channel Enhancement type of MOSFET and explain its working and characteristics. (05 Marks)</p> <p style="text-align: center;">-----OR-----</p> <p>(b) Draw and explain the construction of p-channel Depletion type of MOSFET and explain its working and characteristics. (05 Marks)</p>	[CO4]

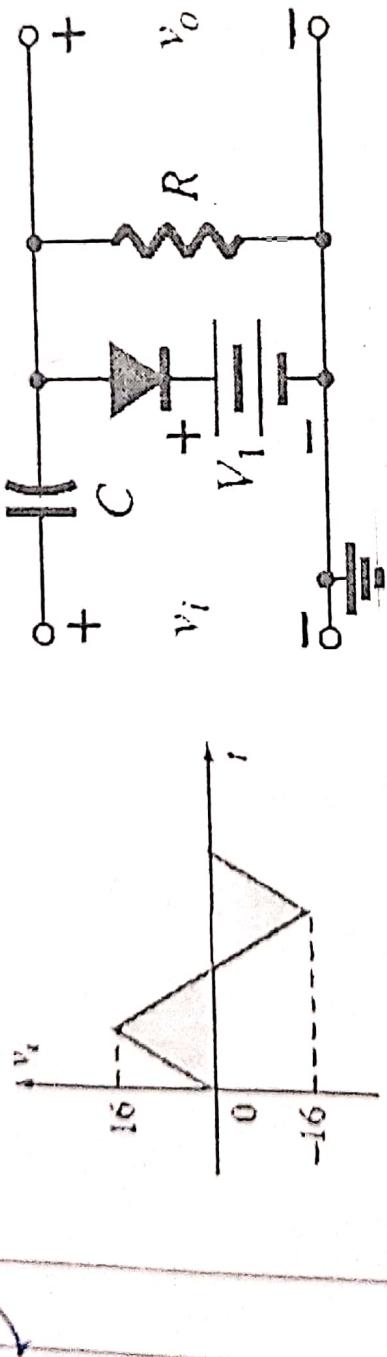- Q4.** (a) Calculate the built-in potential barrier (V_{bi}) in a pn junction. Consider a silicon pn junction at $T = 300$ K with doping concentrations of $N_a = 2 \times 10^{17} \text{ cm}^{-3}$ and $N_d = 10^{15} \text{ cm}^{-3}$.
 (b) For the pn junction diode of Q4(a), what will be the width of depletion region, if a reverse bias voltage of 5 volts is applied to it?
- Q5.** (a) For the following circuit with silicon diode, draw the output waveform
 $(V_1 = 5V)$ and also tell the type of network it is.



- Q6.** Draw the circuit diagram of CE - configuration using pnp transistor and explain its I/O characteristics.
Q7. In the following circuit, find Z_{in} and A_v , if $V_{cc} = +15V$, $R_B = 100 \text{ Kohm}$, $R_E = 100 \text{ Ohm}$, $\beta = 50$.
- Q8.** In the following circuit find V_C and V_B ($R_B = 100 \text{ KOhm}$, $R_C = 1 \text{ KOhm}$ and $\beta = 1.2$)

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA
School of Electronics & Communication Engineering

B. Tech.2nd Semester ECE / Backlog Mid-semester Examination (Even) 2024-25

Entry No:

Date:

Course Title: Solid State Device (ECL DC 102) / Basic Electronics (ECL 1010)

Time Allowed: 1 Hour 30 Minutes


Instructions / NOTE : Attempt All Questions.

- i. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- ii. Assume an appropriate data / information, wherever necessary / missing.


Section - A (5 Marks)

(a) If the reverse saturation current flowing through a pn-junction silicon diode is 20 micro-amperes. Find the forward current flowing through it when a 0.75 V is applied across it at room temperature?

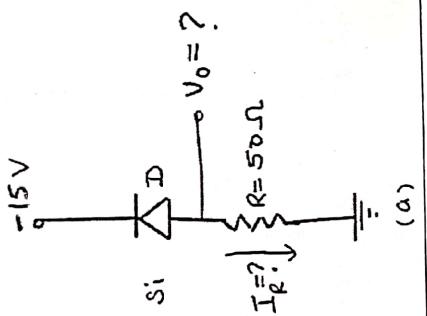(b) Find the current I_R and the voltage V_o in the following circuits?



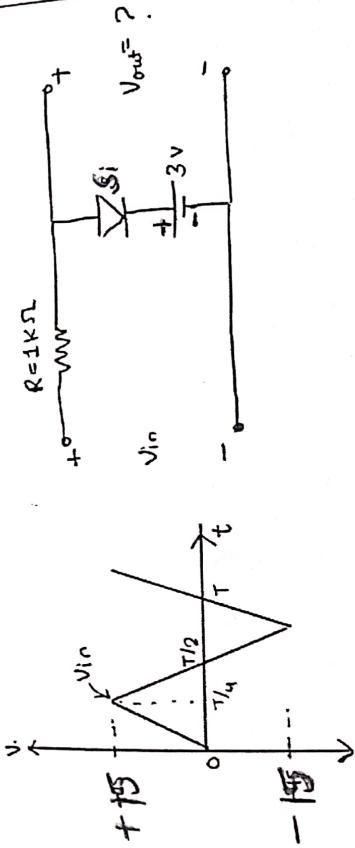(c) Draw the output waveform of the following circuit?



Section - B (15 Marks)

Explain the difference between Avalanche Break-down and Zener Break-down [05] CO1

Draw the circuit diagram of and IO characteristics (with all region of operations) of npn common-base amplifier and explain "Early Effect"? [05] CO1

Draw the bridge rectifier circuit and derive its ripple factor? [05] CO2

OR Explain the working of Zener diode as a voltage regulator.
After successful completion of this course students will be able to achieve this

Course Outcomes

Course Outcome

CO

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA
School of Electronics & Communication Engineering
B. Tech. (ECE) Minor-I Examination, Feb. 2024

Entry No:

--	--	--	--	--	--	--

Total Number of Pages: [01]

Total Number of Questions: [05]

Course Title: Basic Electronics

Course Code: ECL DC102

Time Allowed: 1:00 Hours

Instructions / NOTE

- i. Attempt All Questions.
- ii. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- iii. Assume any missing data to suit the case / derivation / answer.
- iv. Abbreviated terms have their usual meaning.

Q1. Explain the operation of PN junction diode in both biasing schemes with IV characteristics. [4]

Q2. Design a 4-input AND gate using PN junction diodes and explain its operation with truth table. [4]

Q3. A copper wire of 2 mm diameter with conductivity of $5.8 \times 10^7 \text{ s/m}$ and electron mobility of $0.0032 \text{ m}^2/\text{V.s}$ is subjected to an electric field of 20mV/m . Find:

(A) Charge density of free electrons

(B) Current density

(C) Current flowing in the wire

(D) Electron drift velocity.

Q4. Discuss the different diode equivalent circuits with schematic diagrams and IV characteristics. [4]

Q5. A Silicon diode has reverse saturation current of $5\mu\text{A}$ at room temperature. Find the forward bias voltage for a forward bias current of 50mA . [4]

CO:

1. To understand the semi-conductor physics
2. To familiar with PN junction diode and its applications

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA
School of Electronics & Communication Engineering
B. Tech. (ECE) Major Examination, May 2024

Entry No:
Time allowed: 3 Hour

Total Number of Pages: [2]
Total Number of Questions: [8]

Course Title: Basic Electronics
Course Code: ECL DC102

Instructions / NOTE

- i. Attempt All Questions.
- ii. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- iii. Assume any missing data to suit the case / derivation / answer.
- iv. Abbreviated terms have their usual meaning.

Q1. Write the corresponding correct answer with option in your answer sheet. [8]

- I. An electron-Volt (eV) is a unit of _____. (a) Energy (b) Power (c) Charge (d) Momentum
- II. Which element has four valence electrons?
(a) Conductors (b) Insulator (c) Semiconductors (d) None of them
- III. The temperature coefficient of resistance of semiconductors is _____.
(a) Positive (b) Negative (c) Zero (d) Infinite
- IV. A semiconductor in its purest form is called _____.
(a) Pure (b) Doped (c) Intrinsic (d) Extrinsic
- V. The reverse bias diode capacitance is termed as _____.
(a) Diffusion (b) Storage (c) Reverse (d) Transition

VI. _____ is the maximum amount of reverse voltage which can be applied on a diode before breakdown point is reached.
(a) Zener (b) Breakdown (c) PIV (d) Threshold

VII. A _____ is considered as current controlled device
(a) Diode (b) Resistor (c) FET (d) BJT

VIII. What is the barrier potential of Germanium at room temperature?
(a) 0.7V (b) 0.3V (c) 0.5V (d) 0.4V

Q2. Explain the operation of enhancement type NMOS device with input and output characteristics. [6]

Q3. What are the applications of thyristor. How SCR works? Plot the SCR characteristics. [6]

Q4. Find VDS and VGS in the given figure 1, provided that $I_D = 5 \text{ mA}$. [6]

Q5. Derive the expression for stability factor for voltage divider bias scheme. [6]

Q6. Determine Q-point values for the circuit in figure 2 and plot the DC load line. [6]



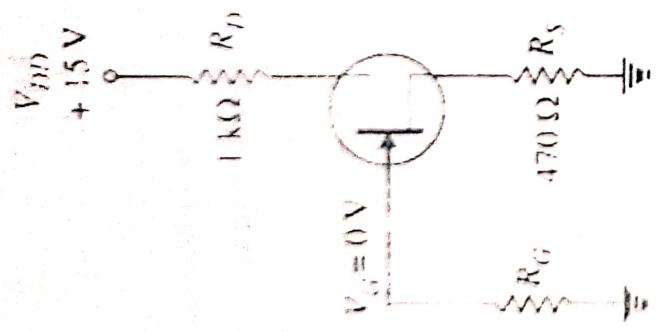


Figure 1

Q7. Explain the hybrid equivalent model for CB configuration of BJT.

[6]
CO
[6]
CO

Q8. What are the criteria for oscillation? Discuss the operation of Wein Bridge oscillator with diagram.

Course Outcomes (COs):

1. To learn the semiconductor devices and applications
2. To understand the characteristics and uses of transistors
3. To learn the biasing schemes and small signal analysis
4. To study the thyristors and oscillators

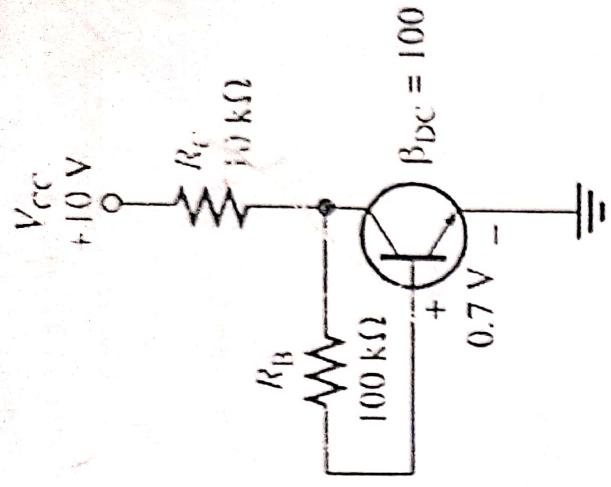


Figure 2

Q8. What are the criteria for oscillation? Discuss the operation of Wein Bridge oscillator with diagram.

[6]
CO
[6]
CO

Entry No:

2	3	v	e	c	o	o	6
---	---	---	---	---	---	---	---

Total Number of Pages: [01]
 Total Number of Questions: [05]
 Course Title: Basic Electronics
 Course Code: ECL DC102

Time Allowed: 1:00 Hours

Instructions / NOTE

- i. Attempt All Questions.
- ii. Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- iii. Assume any missing data to suit the case / derivation / answer.
- iv. Abbreviated terms have their usual meaning.

Q1. Determine V_o , V_1 , I_L and V_2 for the circuit, as given in figure 1 if D_1 is a practical diode: [4]
 CO1

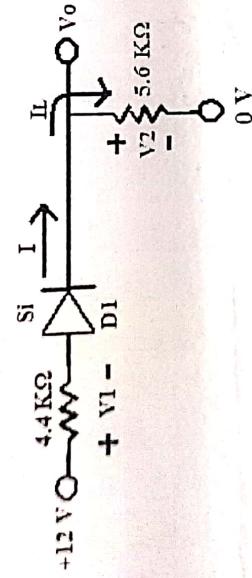


Figure 1

Q2. Explain the operation of CE *n-p-n* transistor with input and output characteristics in detail. [4]

Q3. Derive the expression of input impedance for CE BJT using h-parameter model. [4]

Q4. Determine Q-point values for the circuit, as shown in figure 2. [4]

Q5. Derive the relations among current gains in CE, CB, and CC configurations of BJT. [4]



CO:

1. To understand the applications of diode
2. To understand the fundamentals of BJT

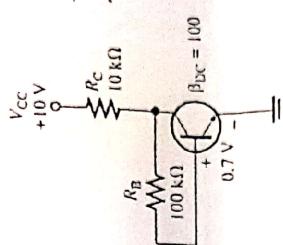


Figure 2

Q2. Explain the operation of CE *n-p-n* transistor with input and output characteristics in detail. [4]

Q3. Derive the expression of input impedance for CE BJT using h-parameter model. [4]

Q4. Determine Q-point values for the circuit, as shown in figure 2. [4]

Q5. Derive the relations among current gains in CE, CB, and CC configurations of BJT. [4]

CO2

SHRI MATA VAISHNO DEVI UNIVERSITY, KATRA
School of Electronics and Communication Engineering
B. Tech. (ECE) Minor I Examination (ODD) 2023-24

Entry No:

2	2	5	2	C	0	8	8	
---	---	---	---	---	---	---	---	--

 Total Number of Pages: [01]
Date: _____

Total Number of Questions: [04]

Course Title: Basic Electronics
Course Code: ECL 1010

Time Allowed: 1.0 Hours Max Marks: [20]

Instructions / NOTE

- Attempt All Questions.
- Support your answer with neat freehand sketches/diagrams, wherever appropriate.
- Assume an appropriate data / information, wherever necessary / missing.


Section - A

Q1.	(i) Number of holes is more than electrons in _____ type of Semiconductor. (ii) In the intrinsic state of the semiconductor, Fermi level resides in _____. (iii) The diode current doubles with the every _____ degree Celsius increase in the temperature. (iv) If the input voltage to the half-wave rectifier is given as $5\sin(2\pi 500t)$ V then average output is _____ V. (v) The load line intersects to the I-V characteristic curve of the diode at _____ point.	[1×5]	CO1 CO1 CO1 CO3
-----	---	-------	--------------------------

Q2. What do you mean by an equivalent circuit model? With the neat diagram, explain different circuit modes of the diode. [05] CO1

Q3. Explain the following terms.
(i) DC Resistance
(ii) Dynamic resistance
(iii) Average resistance

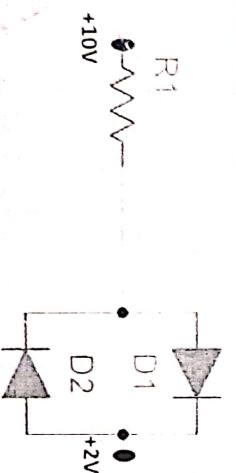Q4. (i) Write a short note on the Zener Diode. What is the use of this diode?
(ii) Determine the direction and the magnitude of the current passing through the diode if $R_1 = 210\Omega$ and diodes are made of Silicon.



Course Outcomes

- To learn basic concepts of semiconductor devices.
- Able to understand and use BJT and MOS Devices
- Learn and able to apply small signal BJT and FET analysis
- To analyze and design rectifiers and amplifiers.
- Able to understand advanced semiconductor devices and oscillators

CO	Questions Mapping	Total Marks	Total Number of Students (to be appeared in Exam)
CO1	1(i),(ii), (iii), 2,3,4(ii)	15	
CO2			
CO3	1(iv),(v),3	05	